

Sommatore a 3 input (v2)

Stefano Scarcelli & Michele De Fusco

27 Dic 2023

Contents

1	Analisi progettuale	3
1.1	Analisi preliminare	3
1.2	Struttura del progetto	3
2	Implementazione	3
2.1	Register n-bit	3
2.1.1	Codice VHDL	3
2.1.2	Sintesi	4
2.2	Three adder (main)	5
2.2.1	Codice VHDL	5
2.2.2	Sintesi	6
2.3	Time constraint	7
2.3.1	Analisi del Time constraint	7
2.4	Risorse	7
2.4.1	Potenza	7
3	Testing	7
3.1	Codice test test-bench	7
3.2	Risultati	10
3.2.1	Simulazione comportamentale	10
3.2.2	Simulazione post sintesi	11
3.2.3	Simulazione post implementazione	12

1 Analisi progettuale

1.1 Analisi preliminare

L'obiettivo è quello di costruire un circuito in grado di sommare 3 numeri a n -bit (*2's complements*) e restituirne il risultato. Sia gli input che gli output devono essere sincronizzati tramite l'uso di registri.

L'idea è quella di usare un sommatore

1.2 Struttura del progetto

La struttura del progetto sarà fatta da un modulo che implementa i **registri** e un'altro dove viene implementato il circuito finale (**Three adder**).

2 Implementazione

2.1 Register n-bit

L'implementazione dell'**Register n-bit** è la medesima del progetto precedente (v1).

2.1.1 Codice VHDL

```
-- Company: UNICAL
-- Engineer: Stefano Scarcelli
--
-- Create Date: 04.12.2023 14:57:11
-- Design Name: ---
-- Module Name: Register_n - Version1
-- Project Name: ThreeNumbersAdder
-- Target Devices: xc7z020clg400-2
-- Tool Versions: 2023.2
-- Description: Parametric n-bit register
--
-- Dependencies: None
--
-- Revision: 1
-- Revision 1.0 - Implementation
-- Additional Comments: ---
--
```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Register_n is
    generic (n : integer := 8);
    Port (CLK, Clear : in STD_LOGIC;
          D : in STD_LOGIC_VECTOR (n-1 downto 0);
          Q : out STD_LOGIC_VECTOR (n-1 downto 0));
end Register_n;

architecture Version1 of Register_n is

begin
    process(CLK, Clear) begin
        if (Clear = '1') then
            Q <= (others => '0');
        elsif rising_edge(CLK) then
            Q <= D;
        end if;
    end process;

end Version1;

```

2.1.2 Sintesi

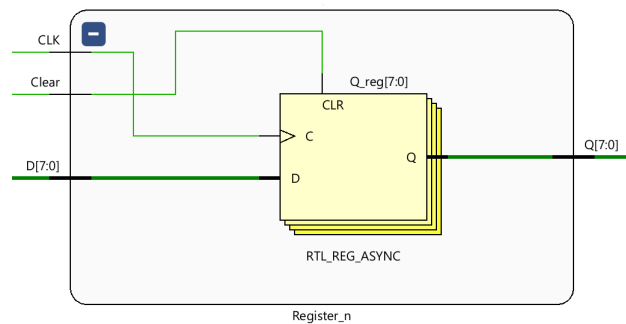


Figure 1: **Registro** a 8bit.

2.2 Three adder (main)

2.2.1 Codice VHDL

```
-- Company: UNICAL
-- Engineer: Stefano Scarcelli , Michele De Fusco
--
-- Create Date: 04.12.2023 15:46:04
-- Design Name: ---
-- Module Name: Three_Adder - Version1
-- Project Name: ThreeNumbersAdder
-- Target Devices: xc7z020clg400-2
-- Tool Versions: 2023.2
-- Description: Main file of the project
--
-- Dependencies: Register_n.vhd, Synched_adder.vhd
--
-- Revision: 1
-- Revision 1.0 - Implementation
-- Additional Comments: ---
--
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Three_Adder is
    generic (n : integer := 8);
    Port (A : in STD_LOGIC_VECTOR (n-1 downto 0);
          B : in STD_LOGIC_VECTOR (n-1 downto 0);
          C : in STD_LOGIC_VECTOR (n-1 downto 0);
          R : out STD_LOGIC_VECTOR (n+1 downto 0);
          CLK : in STD_LOGIC;
          Clear : in STD_LOGIC);
end Three_Adder;

architecture Version1 of Three_Adder is
    component Synched_adder
        generic (n : integer := 8);
        Port (A, B : in STD_LOGIC_VECTOR (n-1 downto 0);
              R : out STD_LOGIC_VECTOR (n downto 0);
              CLK, Clear : in STD_LOGIC);
    end component;
```

```

component Register_n
    generic (n : integer := 8);
    Port (CLK, Clear : in STD_LOGIC;
          D : in STD_LOGIC_VECTOR (n-1 downto 0);
          Q : out STD_LOGIC_VECTOR (n-1 downto 0));
end component;

component Adder
    generic (n : integer := 8);
    Port (A, B : in STD_LOGIC_VECTOR (n-1 downto 0);
          R : out STD_LOGIC_VECTOR (n downto 0));
end component;

signal Rc: STD_LOGIC_VECTOR (n-1 downto 0);
signal Rs,RCext: STD_LOGIC_VECTOR (n downto 0);
signal RSF: STD_LOGIC_VECTOR (n+1 downto 0);

begin
    RCext <= Rc(n-1) & Rc;
    RegC: Register_n generic map(n) port map(CLK, Clear, C, Rc);

    SA1: Synched_adder generic map(n) port map(A, B, Rs, CLK, Clear);
    SA2: Synched_adder generic map(n+1) port map(Rs, RCext, RSF, CLK, Clear);

    RegSF: Register_n generic map(n+2) port map(CLK, Clear, RSF, R);

end Version1;

```

2.2.2 Sintesi

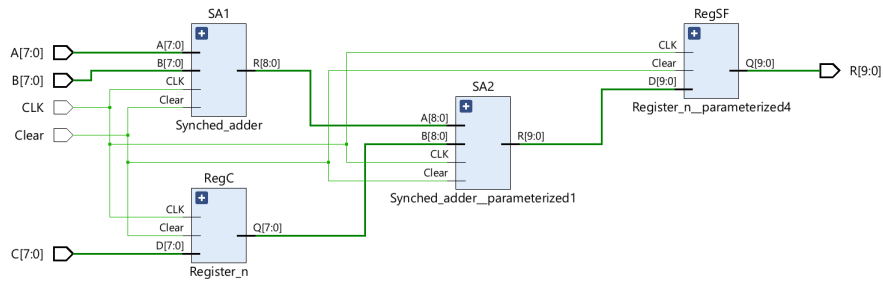


Figure 2: Circuito principale.

2.3 Time constraint

In più abbiamo aggiunto un *time constraint* sul segnale di clock con un periodo di **5ns**.

```
create_clock -period 5.000 -name main_clock
-waveform {0.000 2.500} [get_nets CLK]
```

2.3.1 Analisi del Time constraint

Con l'implementazione del codice abbiamo verificato (*Timing summary routed*) che il **Time constraint** fosse valido, valutando di aver inserito un periodo di clock di superiore rispetto al minimo tollerabile dal circuito di **1.958ns**, rispetto dai **1.958ns** del progetto precedente (v1).

2.4 Risorse

Name	^1	Slice LUTs (53200)	Slice Registers (106400)	Slice (13300)	LUT as Logic (53200)	Bonded IOB (125)	BUFGCTRL (32)
✓ N Three_Adder		17	51	12	17	36	1
<i>I</i> RegC (Register_n)		0	8	3	0	0	0
<i>I</i> RegSF (Register_n_parameterized4)		0	10	5	0	0	0
> <i>I</i> SA1 (Synched_adder)		8	16	8	8	0	0
> <i>I</i> SA2 (Synched_adder_parameterized1)		9	17	9	9	0	0

Figure 3: Risorse usate dai vari componenti.

2.4.1 Potenza

3 Testing

Per il test abbiamo deciso di usare il medesimo test del progetto precedente (v1).

3.1 Codice test test-bench

Resource	Utilization	Available	Utilization %
LUT	17	53200	0.03
FF	51	106400	0.05
IO	36	125	28.80

 


Figure 4: Riassunto delle risorse utilizzate.

```

--- Company:
--- Engineer: Stefano Scarcelli , Michele De Fusco
---
--- Create Date: 12.12.2023 11:20:24
--- Design Name: ---
--- Module Name: Sim_Add - Version1
--- Project Name: ThreeNumbersAdder
--- Target Devices: xc7z020clg400-2
--- Tool Versions: 2023.2
--- Description: Main simulation
---
--- Dependencies: Three_Adder.vhd
---
--- Revision: 2
--- Revision 1.0 - Implementation
--- Additional Comments: ---
---

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_arith.ALL;

entity Sim_Add is
    generic (n : integer := 8);
end Sim_Add;

architecture Version1 of Sim_Add is

```


Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: **0.123 W**
Design Power Budget: **Not Specified**
Process: *typical*
Power Budget Margin: **N/A**
Junction Temperature: **26,4°C**
Thermal Margin: 58,6°C (4,9 W)
Ambient Temperature: 25.0 °C
Effective θ_{JA} : 11,5°C/W
Power supplied to off-chip devices: 0 W
Confidence level: *Low*

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

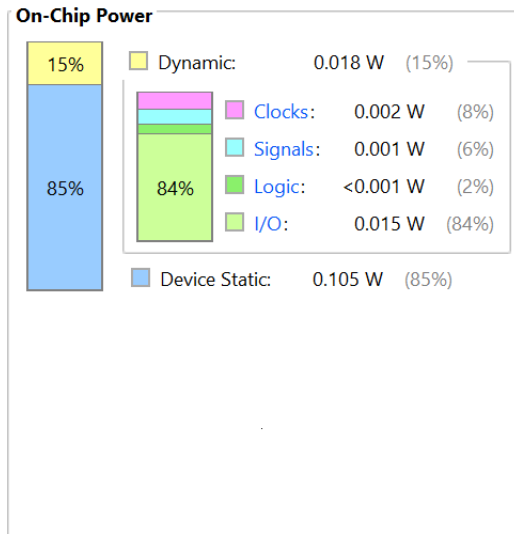


Figure 5: Riassunto del report della potenza del circuito.

```

component Three_Adder
  --generic (n : integer := 8);
  Port (A : in STD_LOGIC_VECTOR (n-1 downto 0);
        B : in STD_LOGIC_VECTOR (n-1 downto 0);
        C : in STD_LOGIC_VECTOR (n-1 downto 0);
        R : out STD_LOGIC_VECTOR (n+1 downto 0);
        CLK : in STD_LOGIC;
        Clear : in STD_LOGIC);
end component;
Signal IA, IB, IC : STD_LOGIC_VECTOR (n-1 downto 0);
Signal ORR : STD_LOGIC_VECTOR (n+1 downto 0);
signal clk, clear : STD_LOGIC;
constant T : time := 10 ns;
begin
  TA : Three_Adder port map(IA, IB, IC, ORR, clk, clear);
  process begin
    clk <= '0';
    wait for T/2;
    clk <= '1';
    wait for T/2;
  end process;

  process begin
    wait for 100 ns;
  end process;
end

```

```

clear <= '1';
wait for T;
clear <= '0';
wait for T/4;

—  $(-1)+(-1)+(-1)=-3$ 
IA <= (others=>'1');
IB <= (others=>'1');
IC <= (others=>'1');
wait for T;

—  $127+127+127=381$ 
IA(n-1) <= ('0');
IA(n-2 downto 0) <= (others=>'1');
IB(n-1) <= ('0');
IB(n-2 downto 0) <= (others=>'1');
IC(n-1) <= ('0');
IC(n-2 downto 0) <= (others=>'1');
wait for T;

—  $(-64)+1+(-63)=0$ 
IA(n-1 downto n-2) <= (others=>'0');
IA(n-3 downto 0) <= (others=>'1');
IB(n-1 downto 1) <= (others=>'0');
IB(0) <= ('1');
IC(n-1 downto n-2) <= (others=>'1');
IC(n-3 downto 0) <= (others=>'0');
wait for T;

— Waiting results
wait for T*2;
end process;

end Version1;

```

3.2 Risultati

I risultati delle simulazioni confermano il funzionamento del circuito come previsto.

3.2.1 Simulazione comportamentale

 


Figure 6: Grafico temporale simulazione comportamentale.

3.2.2 Simulazione post sintesi

 


Figure 7: Grafico temporale simulazione post sintesi.

3.2.3 Simulazione post implementazione

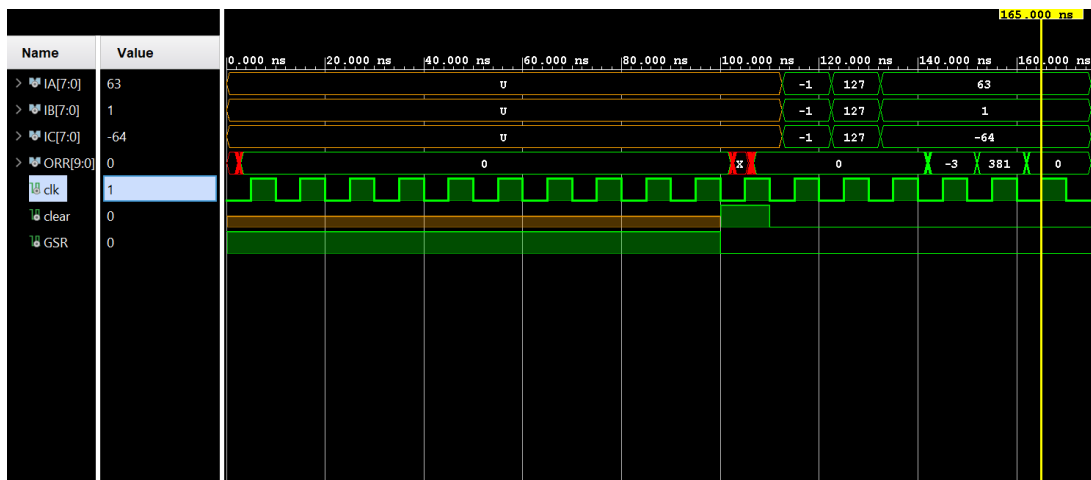


Figure 8: Grafico temporale simulazione post implementazione.